
 


2025 Digital IC Design Homework 1


NAME	童品綸						
Student ID	M16131111						
Functional Simulation Result							
Stage 1	Pass	Stage 2	Pass	Stage 3	Pass	Stage 4	Pass
Stage 1							
# ----- Stage1: Comparator2 Pass ! ----- # # #							
Stage 2							
# ----- Stage2: MedianFinder_3num Pass ! ----- # # #							
Stage 3							
# ----- Stage3: MedianFinder_5num Pass ! ----- # # #							
Stage 4							
# ----- Stage4: MedianFinder_7num Pass ! ----- # # #							
Description of your design							
Stage1 之電路是照助教所給之電路圖時做出找輸入大小的電路，但我的控制訊號只用了一個比較器其實就可以完成，如下圖 schematic。							

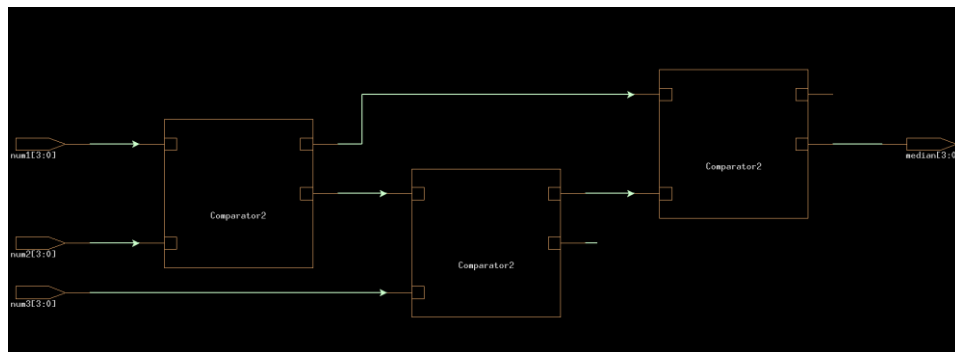


Stage2，則是完全照助教所給電路去 implement RTL code，底下我的 RTL code 之電路 schematic



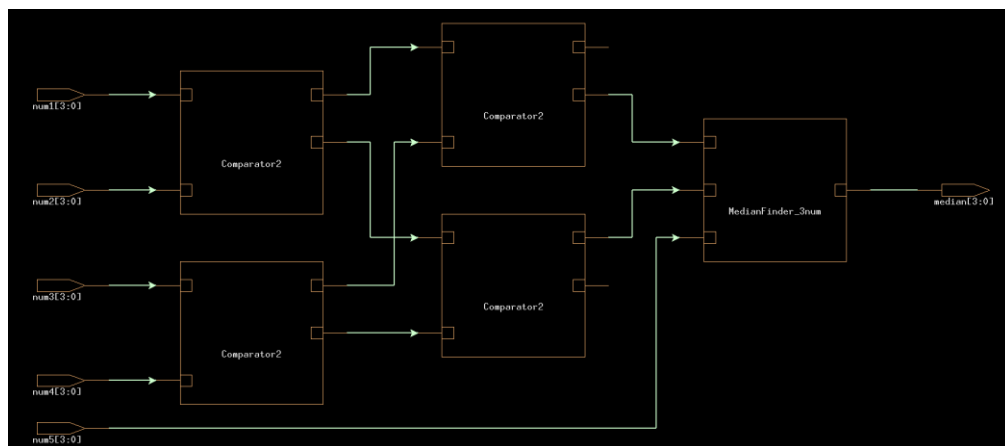
Stage3，也是完全照助教所給電路去 implement RTL code，底下我的 RTL code 之電路 schematic



 Stage4，是照底下的 7-input sort network 來進行改良，由於只要取中間值，所以最後一級的三個比較器實際上只需要一個就可以完成



改良後之 schematic 如下圖

 

而底下為我的 RTL code 之實際 schematic

